

Lab 2 Report

Name: Christian Han

UT EID: cjh3752

Section: 15300

Checklist:

Part 1 –

- i. Simulation waveforms for Part 1 for Structural as well as Behavioral modelling (Screenshots)


Part 2 –

- ii. Truth table of the function
- iii. Algebraic expression of the logic function
- iv. Logic circuit schematic
- v. Verilog codes for module and testbench for structural modelling
- vi. Simulation waveform for structural modelling (Screenshot)
- vii. Verilog codes for module and testbench for behavioral modelling
- viii. Simulation waveform for behavioral modelling (Screenshot)


Note → *The Verilog codes should be copied in your lab report, and the actual Verilog (.v) files need to be zipped and submitted as well on Canvas. You are not allowed to change your Verilog codes after final submission as the TAs may download the submitted codes from Canvas during checkouts. For the truth table, algebraic expression and circuit schematic, you are free to draw it on paper and then put the pictures in your lab report, but please make sure it is legible for the TAs to grade it properly.*



S_1	S_0	I_0	I_1	I_2	I_3	d
0	0	0	x	x	x	0
0	0	1	x	x	x	1
0	1	x	0	x	x	0
0	1	x	1	x	x	1
1	0	x	x	0	x	0
1	0	x	x	1	x	1
1	1	x	x	x	0	0
1	1	x	x	x	1	1

 
 
$$d = s_1' s_0' i_0 + s_1' s_0 i_1 + s_1 s_0' i_2 + s_1 s_0 i_3$$



Structural Module

```
`timescale 1ns / 1ps
module Mux_structural(
    input s1,
    input s0,
    input i0,
    input i1,
    input i2,
    input i3,
    output d
);

//defining wires for not signals
wire s1_not, s0_not;
//defining wires into or gate
wire d0, d1, d2, d3;

//instantiating not gates as per the schematic
not n0 (s0_not, s0);
not n1 (s1_not, s1);

//instantiating and gates as per the schematic
and g0 (d0, i0, s1_not, s0_not);
and g1 (d1, i1, s1_not, s0);
and g2 (d2, i2, s1, s0_not);
and g3 (d3, i3, s1, s0);
or g4 (d, d0, d1, d2, d3);

endmodule
```

Structural Testbench

```
`timescale 1ns / 1ps
```

```
module tb_Mux_structural;
```

```
// Inputs to be defined as registers
```

```
reg s1;
```

```
reg s0;
```

```
reg i0;
```

```
reg i1;
```

```
reg i2;
```

```
reg i3;
```

```
// Outputs to be defined as wires
```

```
wire d;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
Mux_structural uut (
```

```
    .s1(s1),
```

```
    .s0(s0),
```

```
    .i0(i0),
```

```
    .i1(i1),
```

```
    .i2(i2),
```

```
    .i3(i3),
```

```
    .d(d)
```

```
);
```

initial begin

// initialize inputs

s1 = 0;

s0 = 0;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

// wait 50ns for global reset to finish

#50;

s1 = 0;

s0 = 0;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 0;

s0 = 0;

i0 = 1;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 0;

s0 = 1;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 0;

s0 = 1;

i0 = 0;

i1 = 1;

i2 = 0;

i3 = 0;

#50;

s1 = 1;

s0 = 0;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 1;

s0 = 0;

i0 = 0;

i1 = 0;

i2 = 1;

i3 = 0;

#50;

s1 = 1;

s0 = 1;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 1;

s0 = 1;

i0 = 0;

i1 = 0;


i2 = 0;

i3 = 1;

#50;

end

endmodule

 

Behavioral Module

```
`timescale 1ns / 1ps  
module Mux_behavioral(  
    input s1,  
    input s0,  
    input i0,  
    input i1,  
    input i2,  
    input i3,  
    output reg d  
);  
  
    always @(s1, s0, i0, i1, i2, i3)  
    begin  
  
        case ({s1, s0})  
            2'b00 : d = i0;  
            2'b01 : d = i1;  
            2'b10 : d = i2;  
            2'b11 : d = i3;  
        endcase  
  
    end  
  
endmodule
```

Behavioral Testbench

```
`timescale 1ns / 1ps
```

```
module tb_Mux_behavioral;
```

```
// Inputs to be defined as registers
```

```
reg s1;
```

```
reg s0;
```

```
reg i0;
```

```
reg i1;
```

```
reg i2;
```

```
reg i3;
```

```
// Outputs to be defined as wires
```

```
wire d;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
Mux_behavioral uut (
```

```
    .s1(s1),
```

```
    .s0(s0),
```

```
    .i0(i0),
```

```
    .i1(i1),
```

```
    .i2(i2),
```

```
    .i3(i3),
```

```
    .d(d)
```

```
);
```

initial begin

// initialize inputs

s1 = 0;

s0 = 0;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

// wait 50ns for global reset to finish

#50;

s1 = 0;

s0 = 0;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 0;

s0 = 0;

i0 = 1;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 0;

s0 = 1;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 0;

s0 = 1;

i0 = 0;

i1 = 1;

i2 = 0;

i3 = 0;

#50;

s1 = 1;

s0 = 0;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 1;

s0 = 0;

i0 = 0;

i1 = 0;

i2 = 1;

i3 = 0;

#50;

s1 = 1;

s0 = 1;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 0;

#50;

s1 = 1;

s0 = 1;

i0 = 0;

i1 = 0;

i2 = 0;

i3 = 1;

#50;

end

endmodule

